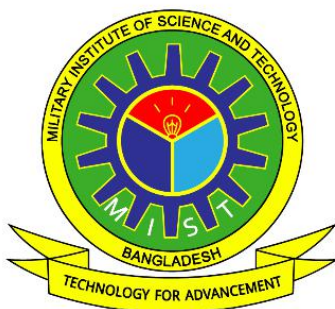


Military Institute of Science and Technology

Department of Electrical Electronic and Communication Engineering

Course: EECE - 314 Electrical Measurement ,Instrumentation

And Sensors Lab



Project Report

Project Name: Inductance Meter Using 555 Timer IC

Group: 01

Group Members	
Name	ID
Labib Siddique Siam	202216025
Md. Faizul Islam Leon	202216038
Md. Mahidul Haque Mahi	202216043
Syed Md Hasin Tasnim	202216301
Md. Rakibul Hasan	202216051
Md. Salman Rashid Himel	202116169

Contents

Abstract.....	02
I. Introduction	03
II. Objective.....	03
III. Methodology:.....	04
A. Theoretical Discussion:	04
B. NE555 IC:.....	08
C. Astable State:.....	10
D. Proteus Simulation:.....	12
IV. Results and Findings:.....	12
V. Discussion:.....	14
VI. References:.....	15

Abstract

This project presents a novel approach to measuring inductance using a 555 timer integrated circuit (IC). The 555 timer, renowned for its versatility in various electronic applications, is employed in this design to generate a specific frequency signal. The inductance to be measured is then incorporated into an oscillator circuit, modifying the frequency of the generated signal. By analyzing the change in frequency, the inductance value can be accurately determined.

The proposed method offers several advantages, including its simplicity, cost-effectiveness, and high accuracy. The 555 timer's inherent characteristics, such as its low power consumption and wide operating voltage range, make it suitable for a broad range of inductance measurement applications.

This project report delves into the theoretical underpinnings of the inductance meter, the circuit design process, and the experimental results obtained. The findings demonstrate the effectiveness of the proposed approach in accurately measuring inductance values within a specified range. This method provides a practical, hands-on solution for learning inductance measurement, making it especially useful for students or hobbyists who may not have access to advanced tools like LCR meters. It not only simplifies the process but also allows for a deeper understanding of the relationship between frequency and inductance. The project highlights how frequency adjustments influence the behavior of inductive components, offering flexibility in design and experimentation. Furthermore, it demonstrates the adaptability of the 555 timer, making it a valuable tool for a variety of low-cost, efficient electronic projects. The simplicity of the 555 timer configuration also encourages users to explore further enhancements, such as improving accuracy through better component selection or using different circuit setups. This project opens opportunities for future work, including integrating the design into more complex systems for enhanced functionality, making it a versatile tool in the field of electronics education and experimentation.

Introduction

Inductance is a key electrical characteristic that defines the capacity of a conductor to store energy within a magnetic field. Precise inductance measurement is essential in many areas, such as electronics, electrical engineering, and physics. Traditional inductance measurement techniques often involve intricate laboratory setups and specialized instruments. This project seeks to create a simple yet effective inductance meter using the versatile 555 timer integrated circuit (IC).

The 555 timer IC is widely recognized for its adaptability in various electronic circuits. Its ability to produce accurate timing signals, coupled with its low power requirements, makes it a suitable choice for this project. By integrating the 555 timer into an oscillator circuit and analyzing the resulting frequency, we can reliably calculate the inductance of an unknown component.

In this report, we will explore the theoretical foundations of the proposed inductance meter, including the workings of the 555 timer, the oscillator circuit design, and the mathematical relationship between inductance and the measured frequency. We will also outline the experimental setup and present the findings, illustrating the accuracy and dependability of the constructed meter.

Objective

The primary objectives of this project report are:

1. To design and implement a functional inductance meter using a 555 timer integrated circuit.
2. To analyze the performance of the proposed inductance meter in terms of accuracy, precision, and sensitivity.
3. To compare the developed inductance meter with existing methods and evaluate its advantages and limitations.
4. To provide a practical guide for constructing and utilizing the 555 timer-based inductance meter.

Apparatus list

- A 555 Timer IC (e.g., NE555 or LM555),
- An unknown inductor for testing,
- Some known capacitor (between 1 nF and 100 nF, ideally with low tolerance),
- Potentiometer (20k Ω for basic circuit needs),
- An oscilloscope or a frequency counter for output frequency measurement,
- A breadboard and jumper wires for assembly,
- A power supply (5V to 12V DC),
- A multimeter (optional for verification).

Methodology

Theoretical Discussion

Inductance is a property of an electrical component, typically a coil or solenoid, that opposes changes in current. It is measured in henries (H). When a current flows through an inductor, a magnetic field is generated around it. If the current changes, the magnetic field also changes, inducing a voltage in the inductor that opposes the change in current.

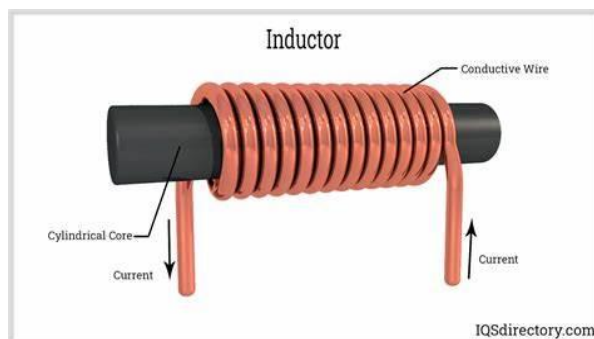


Fig.1: Inductor

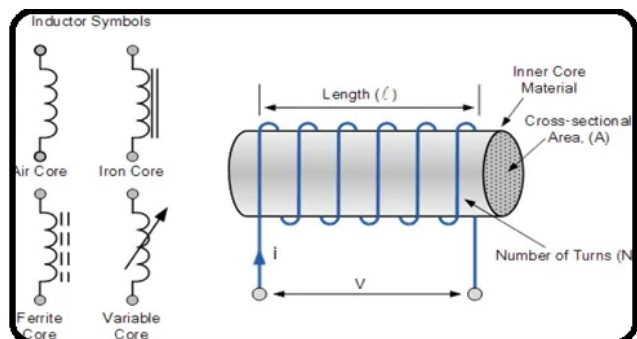


Fig.2: Working Principle of Inductor

Using Inductive Reactance to Determine Inductor's Value

To measure inductance using the 555 timer involves the concept of inductive reactance (X_L). Inductive reactance is a property of an inductor that opposes changes in current flow and is influenced by both the inductance value and the frequency of the AC signal applied to the inductor.

Inductive Reactance Formula

Inductive reactance is calculated using the following equation:

$$X_L = 2\pi fL$$

Where:

- X_L is the inductive reactance (in ohms),
- F is the frequency of the oscillating signal (in hertz),
- L is the inductance (in Henries),
- π is a mathematical constant (approximately 3.14159).

To find the inductance, rearrange the formula to solve for L :

$$L = \frac{X_L}{2\pi f}$$

By determining the inductive reactance X_L and measuring the frequency, the inductance can be calculated.

Relationship Between Reactance and 555 Timer Frequency

In the 555 timer's astable configuration, the output frequency depends on external components, including resistors and capacitors. When an inductor is incorporated into the circuit, it changes the frequency due to its inductive reactance. The total impedance of the circuit—comprising both resistive and reactive elements—determines the oscillation frequency.

By measuring the output frequency of the 555 timer and knowing the circuit's characteristics, you can calculate the inductive reactance of the inductor.

Practical Method for Measuring Inductance

1. **Set Up the 555 Timer Circuit:** Configure the 555 timer in astable mode, ensuring that the inductor is integrated into the timing circuit.
2. **Measure the Oscillation Frequency:** Using a frequency counter or oscilloscope, determine the frequency (F) of the timer's output.
3. **Find the Inductive Reactance:** Estimate the inductive reactance X_L , which is related to the circuit's impedance. You can calculate this using known resistance values and the measured frequency.
4. **Calculate the Inductance:** Once X_L is known, use the below formula to compute the inductance value.

$$L = \frac{X_L}{2\pi f}$$

Important Considerations

- **Measurement Accuracy:** The precision of the inductance measurement depends on the accuracy of the frequency measurement and the estimation of X_L .
- **Circuit Parasitics:** Parasitic inductances and capacitances can affect the measurement, so careful circuit design is important to minimize errors.

- **Component Tolerances:** Variations in resistor and capacitor values can also affect the final result, making calibration essential for improved accuracy.

555 Timer IC

The 555 timer integrated circuit (IC) is a highly versatile component that is extensively used in numerous electronic applications. Initially developed by Signetics in the early 1970s, it has since gained widespread popularity as a reliable and essential element in many circuits.

Key Features and Functions:

- **Timer:** It functions either as a monostable multivibrator (one-shot) or an astable multivibrator (oscillator).
- **Comparator:** The IC includes two comparators that compare the input voltage with two reference voltages.
- **Flip-Flop:** This controls the output state by toggling between high and low based on input conditions.
- **Output Driver:** A transistor or MOSFET is utilized to manage the output signal.

Modes of Operation:

The 555 timer operates in three distinct modes:

1. **Astable Mode**
2. **Monostable Mode**
3. **Bistable Mode**

Working Principle:

Internally, the 555 timer is made up of a voltage divider, comparators, a flip-flop, and an output transistor.

- **Voltage Divider:** This sets the reference voltages for the comparators.
- **Comparators:** They compare the input signals (either the trigger voltage or the voltage across the capacitor) with the reference levels.
- **Flip-Flop:** The flip-flop determines the output state. When the trigger input drops below the lower reference voltage, it sets the output to high. When the capacitor voltage reaches the upper reference voltage, the output is reset to low.
- **Output Transistor:** The output transistor manages the signal at the output pin, switching it between high and low based on the flip-flop's state.

Applications:

- **Timers and Delays:** Used for generating time delays, pulse generation, and sequential timers.
- **Oscillators:** Can be used to create square, triangular, and other waveforms.
- **Voltage Regulation:** Helps in regulating voltage levels in circuits.
- **Pulse Width Modulation (PWM):** Controls the duty cycle of pulses in various applications.
- **Digital Circuits:** Useful for implementing digital logic functions.

Advantages:

- **Versatility:** Applicable across a broad range of electronic projects.
- **Reliability:** A well-established and trusted component.
- **Affordability:** Low cost, making it accessible for many users.

- **Ease of Use:** Simple in design, making it easy to implement and understand.

The 555 timer IC is a staple in the toolkit of both professional engineers and hobbyists due to its versatility, reliability, and ease of use in a wide variety of electronic designs.

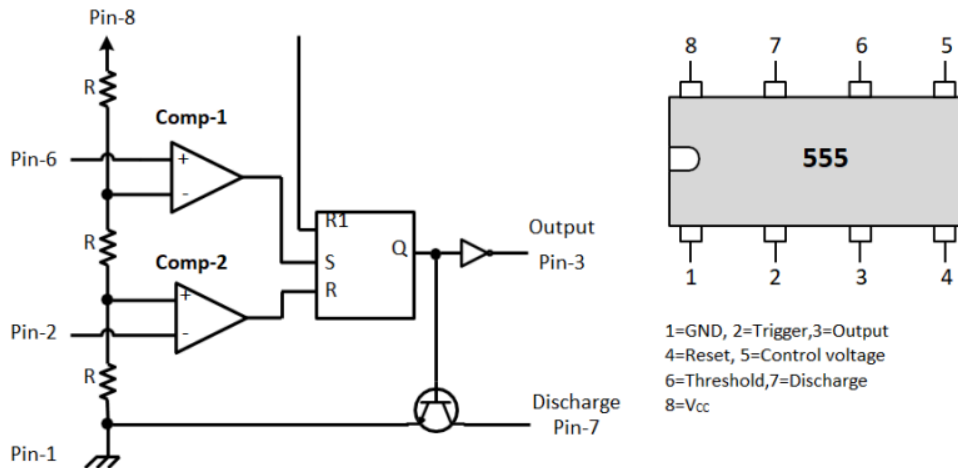


Fig.3: Internal Diagram of NE555

Astable Mode

In the astable mode, the 555 timer functions as a free-running oscillator that continuously generates a square wave signal without needing any external triggering. This means the output switches between high and low states at regular intervals, producing a consistent oscillating signal.

The frequency and duty cycle of the output waveform are controlled by the external components connected to the 555 timer, specifically two resistors (R1 and R2) and a capacitor (C1). These components determine how long the output remains in its high and low states during each cycle.

Working Principle:

- The capacitor (C1) charges through both resistors, R1 and R2, and discharges only through R2. This charging and discharging process sets the

timing for how long the output stays high (during charging) and how long it stays low (during discharging).

- When the voltage across the capacitor reaches two-thirds of the supply voltage, the output switches from high to low, and the capacitor begins to discharge. Once the voltage drops to one-third of the supply voltage, the output switches back to high, and the capacitor starts charging again.
- This continuous process creates a square wave with a frequency determined by the resistor and capacitor values, following the formula:

$$f = \frac{1.44}{(R_1 + 2R_2)C}$$

Applications:

Astable mode is widely used in applications such as:

- **Pulse generation:** Producing clock signals or timing pulses for digital circuits.
- **Flashing lights:** Used in circuits like blinking LEDs.
- **Tone generation:** Generating sound in alarms or sirens.
- **PWM control:** In modulating the duty cycle for pulse width modulation applications.

The versatility of the 555 timer in astable mode makes it a go-to choice for simple and reliable signal generation in many electronic projects.

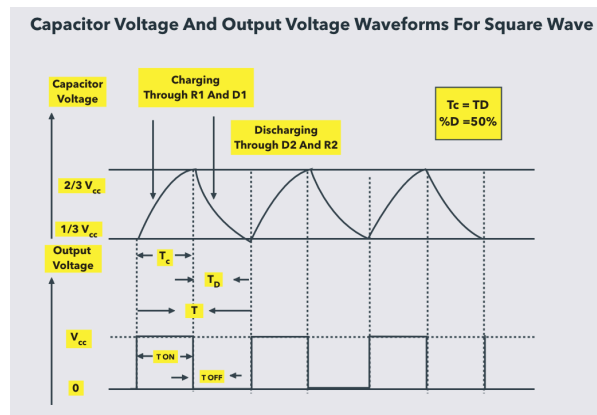
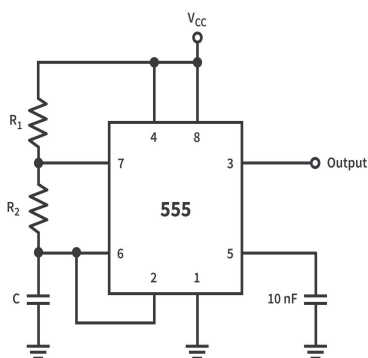


Fig.4: Output of Astable NE555

Proteus Simulation

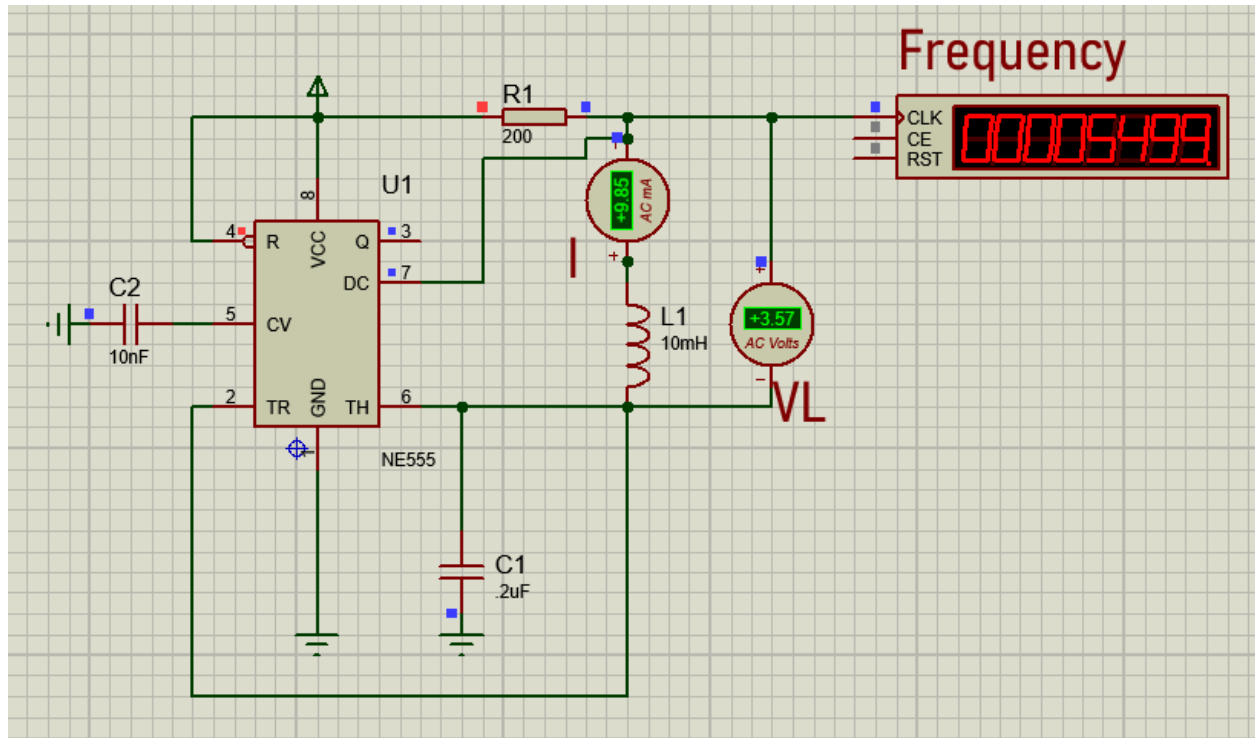


Fig.5: Proteus Simulation

Results and findings

Reactance Calculation

The reactance of an L equation is given by the following formula:

$$L = \frac{X_L}{2\pi f}$$

Where:-

-F is the frequency of the oscillation

- L is the inductance of the inductor
- X_L is the reactance of the inductor

Again, to find the reactance we have,

$$X = \frac{V}{I}$$

Where,

- V is the voltage across the inductor.
- I is the current flowing through the inductor.

Now, as we can see we used 10mH as an unknown inductance and according to it we have a certain frequency. The 1st equation here can solve the problem as the 10mH is unknown. Therefore, to find its reactance we will use the 2nd equation.

From the Simu we have,

$$\begin{aligned} V &= 3.57V \\ I &= 9.85mA \end{aligned}$$

Now, inputting them in equation 2 we have,

$$X_L = \frac{V}{I} = \frac{3.57}{9.85 \times 10^{-3}} = 362.436 \Omega$$

Using this value on equation 1 we get,

$$L_m = \frac{X_L}{2\pi f} = \frac{362.436}{2\pi \times 5499} = 10.5mH$$

Lets see the error,

$$\begin{aligned} \%Error &= \frac{L_m - L}{L} \times 100\% \\ &= \frac{10.5 - 10}{10} \times 100\% \\ &= 5\% \end{aligned}$$

This measurement totally depends on the resistor and the capacitor that was connected with the NE555 IC. However, the error may vary in which type of inductor is used to measure.

Discussion

This is the more or less info and how we can do the measurement of inductance using 555 timer. As this was our 1st open hand project on it we have learned many things. Those are written below :-

1. The Role of Frequency in Inductance Measurement

One crucial aspect of this method is how frequency influences inductance measurement. Since inductive reactance increases with frequency, the 555 timer's output frequency plays a significant role. Higher frequencies result in larger reactance for the same inductor, allowing us to better observe the inductor's properties in different conditions.

This method demonstrates how frequency and inductance are intertwined, providing a clear link between theoretical concepts and practical circuit behavior. By controlling the frequency of the square wave generated by the 555 timer, we can effectively vary and analyze the inductance of different components.

2. Practical Use of the 555 Timer for Inductance Measurement

The 555 timer is a popular and widely available IC, known for its reliability and versatility. Its use in this context offers a practical and affordable way to measure inductance, especially for students or hobbyists who may not have access to specialized equipment like an LCR meter.

In this setup, the 555 timer operates in astable mode, generating a continuous square wave. By configuring the resistors and capacitors that control the frequency, the timer can be tuned to produce a signal at a specific frequency, which then interacts with the inductor in the circuit. This method provides a hands-on learning experience and emphasizes the practical application of theoretical knowledge.

3. Limitations and Accuracy Considerations

While using a 555 timer to measure inductance is practical, it comes with certain limitations. The accuracy of the results depends on the precision of the frequency generated by the 555 timer, as well as the accuracy of the voltage and current measurements. Additionally, the quality of the components used in the circuit can affect the stability of the frequency, which may lead to errors in the inductance calculation.

To improve accuracy, careful selection of resistors and capacitors in the 555 timer circuit is important, as these components influence the stability of the generated frequency. Despite these challenges, the method remains a useful educational tool for exploring the behavior of inductors.

4. Practical and Theoretical Learning

This method of using a 555 timer for inductance measurement offers a practical application of theoretical concepts like inductive reactance and Ohm's Law in AC circuits. It provides a straightforward and accessible way to understand inductors in AC circuits, bridging the gap between classroom theory and real-world applications.

Furthermore, it demonstrates the flexibility of the 555 timer as a tool not just for timing or waveform generation, but also for conducting simple experiments and measurements in electronics. This encourages innovative thinking in circuit design and experimentation.

References

1. Essential 555 IC: Design, Configure, and Create Clever Circuits by Cabe Satalic Atwell
2. Timer, Op Amp, and Optoelectronic Circuits & Projects Paperback – by Forrest M.. Mims III(Author)

3. 555 oscillator tutorial from electronics tutorial.
4. Hyperspace Pirate youtube channel Inductor Tester
5. NE555 Datasheet (PDF) - Texas Instruments
6. 555 Timer IC Pinout, Circuit, Working from electronicsforum website.
7. How to choose the right frequency when measuring coil inductance with LCR meter from electricalengineering.